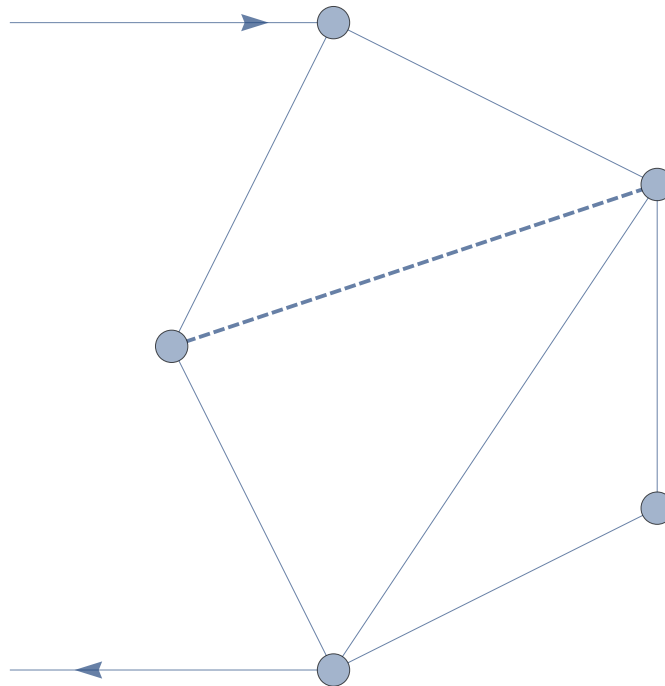


Problem 1. Consider the graph below as an electrical circuit where each edge has resistance 1 and a current of size 1 enters the graph at the source at the top and exits the graph at the sink at the bottom.



- (a) Compute the number of spanning trees. Do it several ways: multiply the nonzero eigenvalues of the Laplacian, compute the determinant of the reduced Laplacian, draw a picture of all of them.
- (b) Determine the current flowing in each edge by using Kirchoff's laws.
- (c) Determine the current flowing in the dotted edge by Theorem 1 in Section II.1 in the book.
- (d) Compute the page ranks for the directed graph obtained by connecting the sink to the source and considering the edges to be directed according to the flow of the current.